




# ٦٠- لاب الكترونيات

٨٠-١



١٣٤

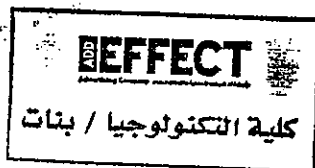

سعر التصوير بدون تغليف : ٧٥٠ فلس  
سعر التغليف : ٥٠٠ فلس  
سعر المذكرة مع التغليف : ١.٢٥٠ دك

7.



Public Authority for Applied Education & Training

College of Technical Studies

Electronics Engineering Department

Electronics I

ENT134

Lab Manual

الالكترونيات  
لـ ب

Prepared by  
Eng. Hussain Bunayan

## Table of Contents

	Page
EXPERIMENT No1: Diode Characteristics	1
EXPERIMENT No 2: Half-Wave Rectifier	4
EXPERIMENT No 3: Full-Wave Rectifier	7
EXPERIMENT No 4: Zener Diode	10
EXPERIMENT No 5: Transistor Self-Biasing	13
EXPERIMENT No 6: BJT Biasing (Voltage Divider Bias)	16
EXPERIMENT No 7: Impedance, Power, and Phase Relationship of Common-Emitter Amplifier	19
EXPERIMENT No 8: The Emitter Follower	23
EXPERIMENT No 9: JFET Common Source Amplifier	27
EXPERIMENT No 10: JFET Common Drain Amplifier	31
EXPERIMENT No 11: Inverting Amplifier	34
EXPERIMENT No 12: Noninverting Amplifier	37
EXPERIMENT No 13: Summing Amplifier	39
EXPERIMENT No 14: Difference Amplifier	44
EXPERIMENT No 15: Comparators	47
EXPERIMENT No 16: Integrator and Differentiator	51
Appendix A: How to use Electronics Workbench	55
Appendix B: Hampden Part List	63

## Experiment No. (1) Diode Characteristics

### Objectives:

To demonstrate **FARWARD** and REVERSE current and voltage characteristics of a "p n" junction diode.

### Theoretical Background:

As forward current ( $I_F$ ) through a diode increases, forward voltage ( $V_F$ ) across does the same. However due to the changing characteristics of the forward biased diode,  $V_F$  will increase at much lower rate than  $I_F$ . When a diode is reverse biased, the reverse current ( $I_R$ ) through the device will be extremely low, even when there is a significant reverse voltage ( $V_R$ ) across the diode. This is due to the extremely high resistance of reverse biased diode.

### Materials and equipment:

- 1- Power Supply.
- 2- AVO meter (analog).
- 1- Small signal Diode.
- 1- Rectifier Diode.
- 1- Resistor 1 k $\Omega$ .

### Procedure:

- 1- Identify the terminals of the diode.
- 2- Use the AVO meter to measure the forward resistance of the diodes, and record in Table (1.1).

Diode number	Forward Resistance	Reverse Resistance

Table (1.1)

- 3- Reverse the diodes and measure the reverse resistance, and record in Table (1.1).
- 3- Set the circuit of Figure (1.1).

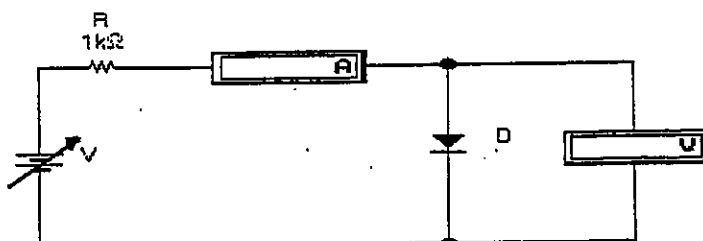


Fig (1.1)

- 4- Increase the voltage so that you have forward current as indicated in Table (1.2), and record the voltage

Forward current(mA)	Forward voltage (v).
0	0
0.5	
1.0	
1.5	
2.0	
3.0	
4.0	
5.0	
6.0	
7.0	
8.0	

Table (1.2)

- 5- Repeat for all other currents, and complete Table (1.2).

- 6- Reverse polarity of the diode as shown in Figure (1.2).

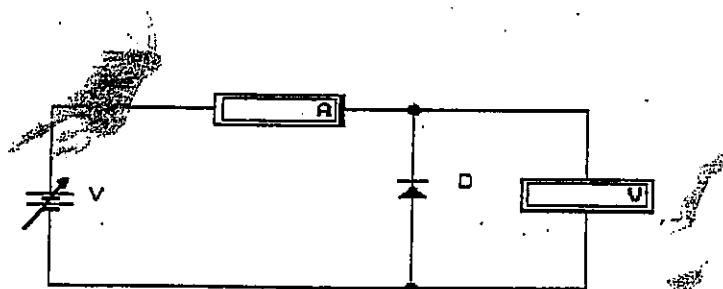


Figure 1.2.

- 7- Increase the reverse voltage as indicated in table (1.3), measure and record reverse current.

Reverse Current ( $\mu\text{A}$ )	Reverse Voltage(V)
	1
	5
	10
	20
	30
	40

Table 1.3

- 8- Using the data you collected in Tables (1.2) and (1.3), plot the points that represents each reading, compare your curve with the one you studied in the lecture.
- 9- Calculate the forward, and reverse resistance  $R_F$ ,  $R_R$  using the equation  

$$R = \Delta V / \Delta I$$
- 10-Discuss in your own words, what you have observed, concluded from this experiment.

## Experiment No. (2) Half-Wave Rectifier

### Objective:

To demonstrate the construction, and operation of half-wave rectifier.

### Theoretical Background:

The half-wave rectifier is the simplest of the rectifier circuits. It converts ac input to pulsating dc by simply eliminating either the positive alternations of the input (for a negative dc power supply), or the negative alternations of the input (for a positive dc power supply).

### Materials and equipment:

- 1-Oscilloscope
- 1-AVO meter (analog).
- 1-Transformer, rated 240 V<sub>ac</sub> input and 12 V<sub>ac</sub> output.
- 1- Si Rectifier Diode (# 547).
- 1- Resistor 5.6 k $\Omega$ .  
(225)

### Part I (Experimental)

#### Procedure:

- 1- Construct the circuit of Figure (2.1).

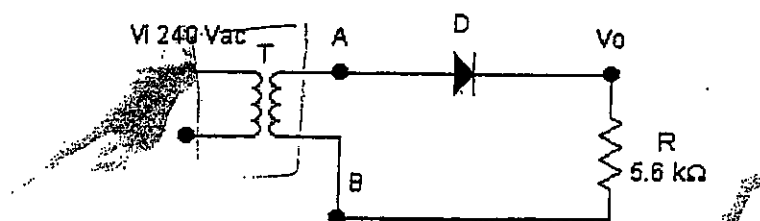


Fig (2.1)

- 2- Apply power to the circuit.
- 3- Measure and record the rms and peak-to-peak voltage as indicated in Table (2.1).
- 4- To calculate the input and output frequencies, measure the input and output time period, record in Table (2.1).

Points	AVO meter	Oscilloscope			
		Ne nF squares	V/Div. T/Div.	Result	Wave-form
$V_{AB}$	***** ***** ***** ***** *****				
$V_o$					
$T_{in}$	***** ***** ***** ***** *****				$f = 1/T$
$T_o$	***** ***** ***** ***** *****				$f = 1/T$

Table 2.1

5- Reverse the diode, and observe the output waveform.

### Part II (Computer Simulation)

Procedure:

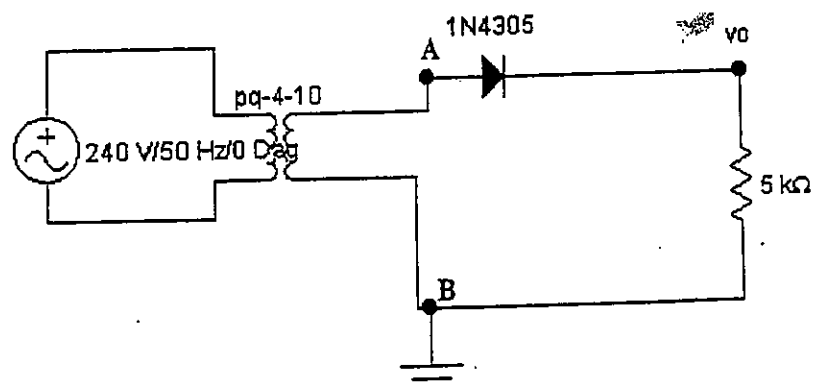


Fig (2.2)



- 1- Setup the circuit of Figure 2.2 using (Electronics Workbench Software).
- 2- Connect the oscilloscope to the input terminals AB, and the output terminals Vo.
- 3- Observe the signal waveforms, and print out, to submit with your report.

### Report

1- Is  $V_{AB(rms)}$  measured =  $\frac{V_{AB(p)}}{\sqrt{2}}$

2- Is the value of  $V_{O(dc)}$  measured = 0.318  $V_p$ ?

3- What is the PIV for the diode used?

4- Write brief conclusion about the main idea of the experiment.

## Experiment No. (3) Full-Wave Bridge Rectifier

### Objective:

To demonstrate the construction and operation of center-tapped transformer full-wave rectifier.

### Theoretical Background:

The full-wave center-tapped rectifier changes ac to pulsating dc by either converting the negative alternations to positive alternations (for positive dc power supply) or by converting the positive alternations of input signal to negative alternations (for a negative dc power supply).

### Materials and Equipment:

- 1-Oscilloscope.
- 1-AVO-meter (analog).
- 1-Transformer, rated  $240\text{ V}_{ac}$  input and  $12\text{ V}_{ac}$  output (6/4)
- 2-Si Rectifier Diode (#547).
- 1-Resistor  $5.6\text{ k}\Omega$

### Part I (Experimental)

#### Procedure:

- 1- Construct the circuit of Figure (3.1).

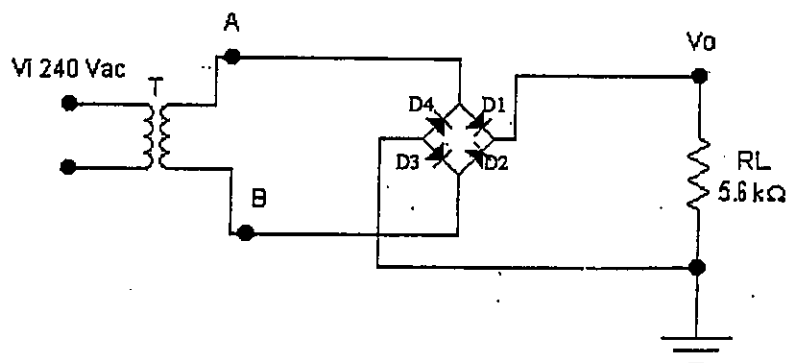


Figure 3.1

- 2- Apply power to the circuit.
- 3- Measure the rms and peak to peak values of the secondary voltage of the transformer  $V_{AB}$  record in Table 3.1.
- 4- Measure the output voltage  $V_o$  as indicated in Table 3.1.
- 5- Remove the load resistor  $R_L$  from the circuit, measure and observe the waveform at point  $V_o$  record in Table 3.1.
- 6- Disconnect power from the circuit and return  $R_L$  to its original position in the circuit. Now, remove  $D_1$  from the circuit and apply power.

7- Observe and measure the output waveform, record in Table 3.1.

8- Measure the time period of the input and output signal.

Points	AVO meter	Oscilloscope			
*****	*****	Number of squares	V/Div. T/Div.	Result	Wave-form
$V_{AB}$					
$V_o$					
$V_o$ No Load $R_L$					
$V_o$ One Diode Remo ved					
$T_{in}$	***** ***** ***** **				$f = 1/T$
$T_o$	***** ***** ***** ***** ****				$f = 1/T$

Table 3.1

## Part II (Computer Simulation)

## Procedure:

- 1- Setup the circuit of Figure 3.2 using (Electronics Workbench Software).

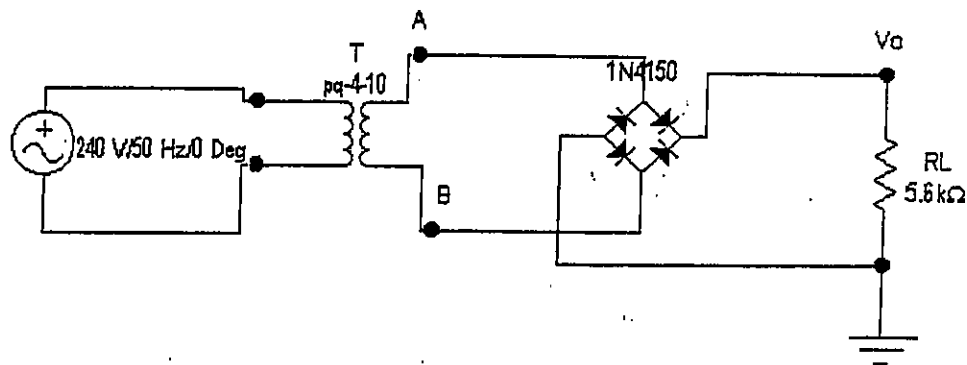


Fig 3.2

- 2- Connect channel 1 of the oscilloscope to the secondary terminals of the transformer A.B observe the waveform.
- 3- Connect channel 2 of the oscilloscope to the output of the rectifier circuit observe the waveform.

## Report:

- 1- Explain why an open load resistor caused the waveform you saw in step 5 of the practical procedure.
- 2- Explain why an open diode in the bridge caused the waveform you saw in step.6 of the practical procedure.
- 3- Is the value of  $V_{O(dc)} = 0.638 V_p$ ?
- 4- What should be the PIV for the diodes used in the experiment?
- 5- Write brief conclusion about the main idea of the experiment.
- 6- Submit a printout of the waveforms in the simulation procedure.

## Experiment No. (4) Zener Diode

### Objectives:

- To demonstrate the constant-voltage characteristics of the Zener diode.
- To introduce zener diode as voltage regulator.

### Theoretical Background:

The zener diode is a component that maintains a relatively constant voltage across its terminals even when there is a relatively large change in device current. The voltage across the terminals is approximately equal to the nominal Zener voltage ( $V_Z$ ) of the component as long as the device current stays within a specified range. The typical tolerance in terminal voltage is  $\pm 20\%$ .

A constant dc output voltage is what we seek from regulated power supplies, to do this a zener is used to adjust it self from variation of input source or load resistance which causes the change in voltage level.

### Materials and Equipment:

- 1-Power supply.
- 1-AVO-meter (analog).
- 1-Resistor  $100\ \Omega$ .
- 1-Zener diode(# 531).
- 1- Resistor  $500\ \Omega$ .
- 1- Digital voltmeter.
- 1- Resistor Box.

### Part A (Zener Diode Characteristics)

#### Procedure:

- 1- Construct the circuit shown in Figure (4.1).

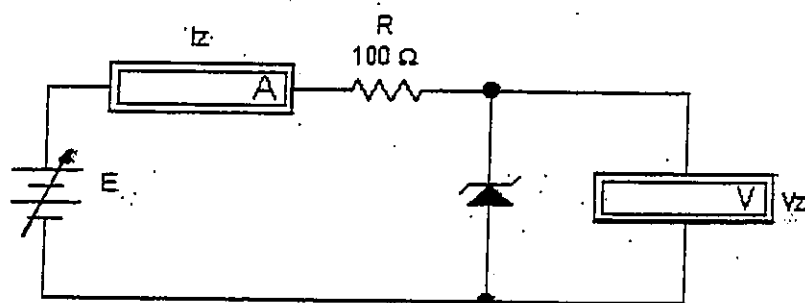


Figure 4.1

- 2- Apply power to the circuit, increase the voltage  $E$  until  $V_Z$  equals  $1\text{V}$  measure  $I_Z$ , and record its value in Table (4.1).
- 3- Repeat for the other values of  $V_Z$  as indicated in Table (4.1); measure and record as you did in step 2.

Zener	Zener

Table 4.1

**PART B (ZENER DIODE REGULATOR)****(With Varying Source & Constant Load Resistance)****Procedure:**

- 1- Construct the zener diode regulator circuit of Figure (4.2), set the resistance box to  $1\text{ k}\Omega$ .

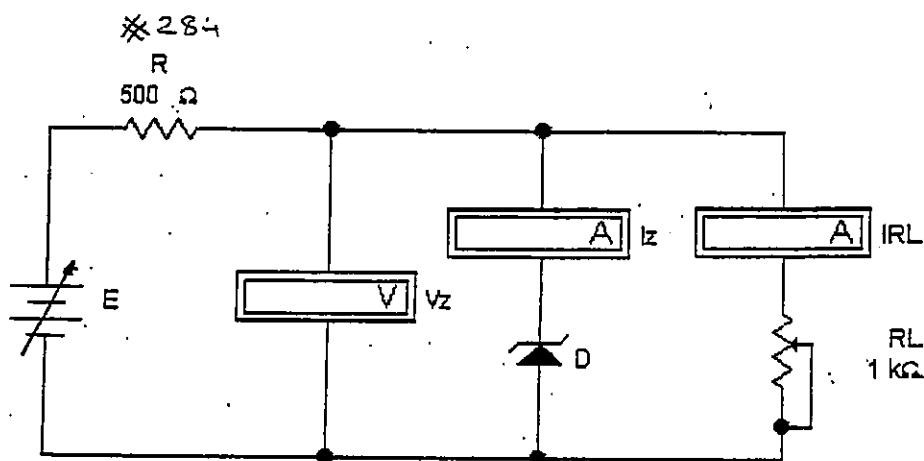


Figure 4.2

2- Increase the voltage as indicated in Table (4.2), measure  $V_z$ ,  $I_z$ ,  $I_L$  and record in the proper spacing.

E (v)	0	2	4	6	8	10	12	14	16	18	20
$V_z$ (v)											
$I_z$ (mA)											
$I_L$ (mA)											

Table 4.2

3- We know  $V_z$  from part (A), otherwise ask your instructor. Calculate the value of E at which the zener diode should be on using the equation.

$$E = V_{z(on)} \frac{R + R_L}{R_L} \rightarrow$$

(With Varying load & Constant input Source)

4- With the same circuit of Figure (4.2), hold the input voltage constant at 18.5 v.

5- Increase the resistance of resistance box as indicated in Table (4.3), measure and record  $V_z$ ,  $I_z$ , and  $I_L$  in the proper spacing.

Resistance box ( $R_L$ )	100 $\Omega$	300 $\Omega$	500 $\Omega$	700 $\Omega$	900 $\Omega$	1000 $\Omega$	1200 $\Omega$
$V_z$							
$I_z$							
$I_L$							

Table 4.3

### REPORT:

1- Plot the data in Table 4.1

2- Calculate the right value of  $R_L$  so that the zener diode will be on (use voltage divider rule).


3- What is the limitation of zener diode regulator circuit?

4- Write brief conclusion about the main idea of the regulator part of the experiment?

## Part I (Experimental)
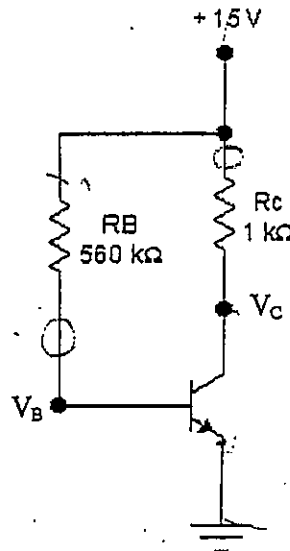
## Procedure:

- 1- Connect the circuit shown in Figure 5.1.



*Handwritten notes:*  
 PPT  
 R<sub>B</sub> not R<sub>E</sub>

*Note* start table 5.2 then 5.1

Figure 5.1

- 2- With your AVO-meter, measure the currents through the base and collector resistors, record your values in Table 5.1. From these two sets of values, determine the dc current gain, or beta ( $\beta_{dc}$ ), record in Table 5.1.
- 3- Measure  $V_B$  and  $V_{CEQ}$ . Record in Table 5.1.
- 4- Now carefully place a soldering iron near the transistor for a few seconds while measuring the collector current using your AVO-meter. Does the collector increase or decrease?
- 5- Disconnect power from the circuit and replace the 560-k $\Omega$  resistor ( $R_B$ ) with a 1-M $\Omega$  potentiometer. Again apply power to the circuit and connect a voltmeter between the transistor's collector terminal and ground.
- 6- Now vary the resistance of the potentiometer until  $V_{CE}$  as read by the voltmeter reaches a minimum value,  $V_{CE(sat)}$ . Then measure the corresponding collector current,  $I_{C(sat)}$ . Record both values in Table 5.2.
- 7- Continue to vary the resistance of the 1-M $\Omega$  potentiometer until  $V_{CE}$  reaches a maximum value,  $V_{CE(off)}$ . Then measure the corresponding collector current  $I_{C(off)}$ , record both values in Table 5.2.
- 8- Vary the potentiometer so that you are able to measure about five combinations of  $I_C$  and  $V_{CE}$  over the active region of the dc load line, recording all values in Table 5.2.



## Experiment No. (5)

### Transistor Self-Biasing

#### Objectives:

- To study the transistor three states: Saturation, active and cutoff.
- To study the effect of  $\beta$  and temperature on transistor's Q-point under active state.

#### Theoretical Background:

Self-bias is the simplest of the transistor biasing circuit. It consists of single transistor, two resistors, and a power supply.

It would seem that the simplicity of the self-bias circuit would make it ideal for most applications. However, the self-bias circuit is relatively unstable. That is, the Q-point of the circuit will shift (change) if there is a significant change in  $\beta$  and/or temperature. This point will be demonstrated in this experiment. The following equations could be a great help to be able to calculate:

$$V_B = V_{CC} - I_{BQ}R_B = V_{BE}$$

$$I_{CQ} \approx \frac{V_{CC} - V_{BE}}{R_B / \beta}$$

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B}$$

$$V_{CEQ} = V_{CC} - I_{CQ}(R_C)$$

For the dc load line

$$I_{C(sat)} \cong \frac{V_{CC}}{R_C} \quad (\text{Saturation})$$


$$V_{CE(off)} = V_{CC} \quad (\text{Cutoff})$$

And  $\beta$  can be calculated by

$$\beta_{dc} = \frac{I_{CQ}}{I_{BQ}}$$

#### PINNING

PIN	DESCRIPTION
1	collector
2	base
3	emitter

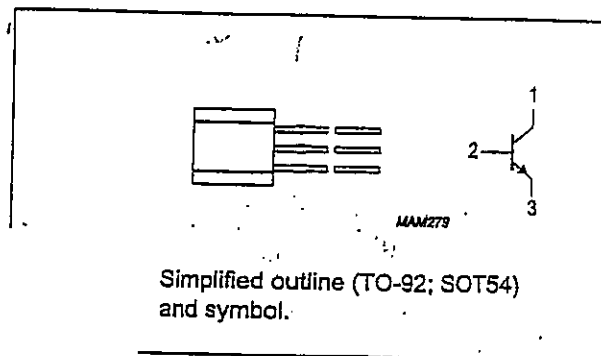

#### Materials and Equipment:

- 1- Power supply.
- 1- AVO meter or digital multi-meter.
- 1- Transistor npn (# 568 or 571).
- 1- Resistor, 1 k ohm.
- 1- Resistor, 560 ohm.
- 1- Potentiometer, 1 M ohm.

## Part II (calculation)

- 1- Calculate the values of  $I_{BQ}$  and  $I_{CQ}$  record in Table 5.1.
- 2- Calculate the value of  $V_{CEQ}$  record in Table 5.1.
- 3- Calculate the saturation and cutoff on dc load line record in Table 5.2.

Note use  
Measured  
 for Calculated

Parameter	Measured Value	Calculated Value
$I_{BQ}$	0.026 mA	
$I_{CQ}$	3.5 mA	
$\beta_{dc}$		
$V_{BE}$	0.7	0.7
$V_{CEQ}$	11.5 V	

$$I_C = \beta I_B$$

X

$$V_{CE} = V_{CC} - I_C R_C$$

Table 5.1

Condition	Calculated Value		Measured Value	
	$I_C$	$V_{CE}$	$I_C$	$V_{CE}$
Saturation (Step 6)	15 V	0		
Cutoff (Step 7)	0	15 V		
Active Region (Step 8)	1.5 mA	13.5 V		
	3	12		
	6	9		
	8	7		
	9	6		

$R_B$

Table 5.2

## Report:

- 1- Plot the calculated point of Table 5.2 on a graph paper.
- 2- Draw the dc load line, and locate saturation and cutoff.
- 3- To what extent the measured and the calculated value are identical.
- 4- Explain the effect of heating the transistor on Q-point and  $\beta$ .
- 5- Write brief conclusions about what you have learned from this experiment.

## Experiment No. (6) BJT Biasing (Voltage-Divider Bias)

### Objective:

To demonstrate the operation of the voltage-divider bias circuit, and the Q-point stability.

### Theoretical Background:

The voltage-divider bias circuit is the most commonly used of the BJT biasing circuit for several reasons:

- 1- It provides excellent operating point stability even with wide change in  $\beta$  and temperature.
- 2- It requires only one power supply voltage.
- 3- It provides a degree of stability with respect to change in supply voltage.

The following equations could be a great help to be able to calculate:

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = 12 \text{ V}$$

$$V_E = V_B - V_{BE}$$

$$I_E = \frac{V_E}{R_E} \quad 18 \text{ mA}$$

$$I_{CQ} \cong I_E$$

$$V_{CEQ} = V_{CC} - I_E (R_C + R_E)$$


### Materials and Equipment:

- 1-Power supply.
- 1-AVO-meter (analog).
- 1-Digital multi-meter.
- 2-Transistor npn (# 568 or 571)
- 1- Resistor 560  $\Omega$
- 1-Resistor 1.5 k $\Omega$
- 1-Resistor 6.8 k $\Omega$
- 1-Resistor 33 k $\Omega$
- 1-Potentiometer 25 k $\Omega$

### Part I (Experimental)
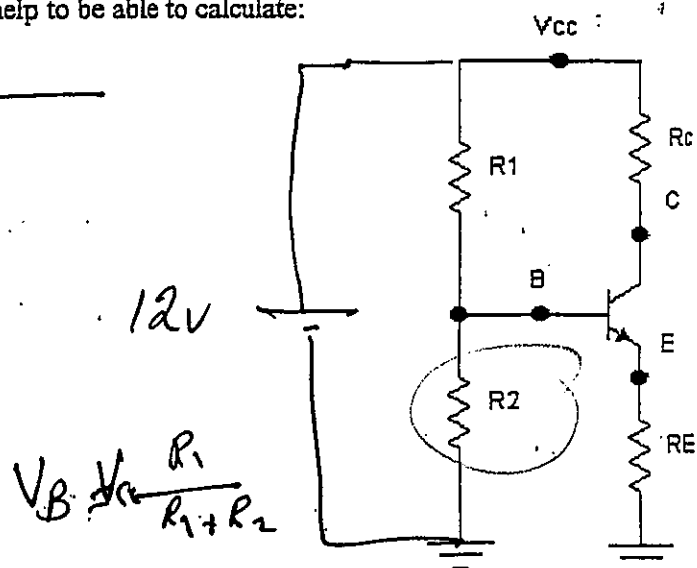
#### Procedure:

- 1- Set the potentiometer to 18 k $\Omega$  (use AVO-meter).
- 2- Construct the circuit of Figure (6.1).
- 3- Now apply 12 volts to the circuit, measure and record the points indicated in Table 6.1
- 4- Adjust  $R_a$  until  $V_B$  is approximately equals the value calculated in part III step 1, repeat the measurements instep (3).



$R_a = 18k\Omega$

	Calculation	$V_B$ <i>2.1</i>
$V_B$	3.2	1.8
$V_E$	2.59	1.15
$V_{BE}$	0.7	0.668
$V_C$	5.07	9.5
$V_{CE}$	2.48	<del>8.39</del> <i>2.39</i>
$I_E$	4.6mA	<i>2mA</i>

*2.39*

$$V_B = \frac{R_2}{R_2 + R_1} V_{CC} = \frac{6.8}{18 + 6.8} 12 = 3.2$$


$$I_C R_C = 4.5 \times 1.5$$

$$= 6.93$$

for  $I_C \approx I_E$

$$-V_{CC} + I_C R_C + V_C = 0$$

$$V_C = 5.07$$

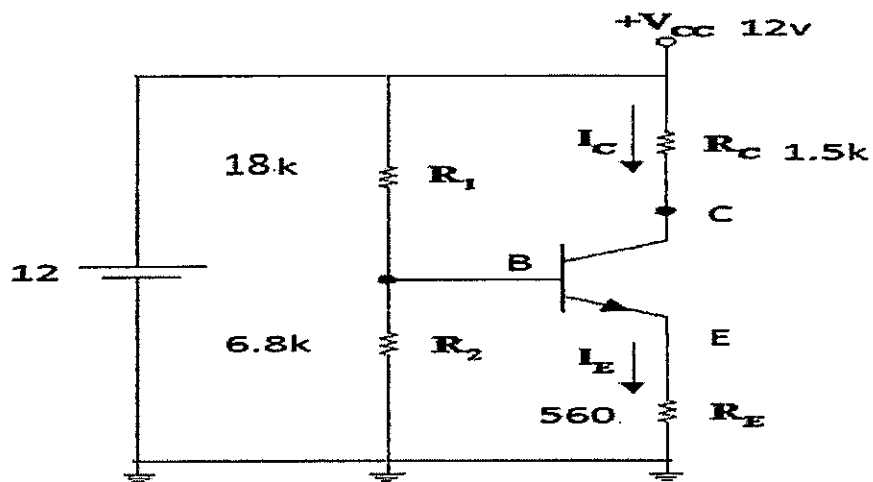

	Calculation
$V_B$	1.9
$V_E$	1.2
$V_{BE}$	0.7
$V_C$	9
$V_{CE}$	7.8
$I_E$	2 mA

$$V_B = \frac{R_2}{R_2 + R_1} V_{CC} = \frac{6.8}{36 + 6.8} 12 = 1.9$$


$$I_C R_C = 2 \times 1.5$$

$$= 3$$

$$\text{for } I_C \approx I_E$$

$$-V_{CC} + I_C R_C + V_C = 0$$

$$V_C = 9$$

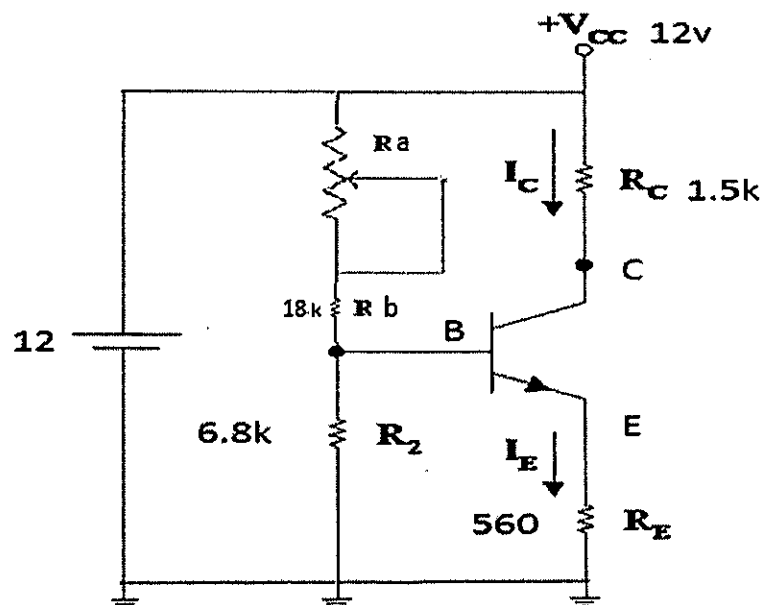

نیم تغییر یافته و به صورت  $V_B = 1.9$  می شود

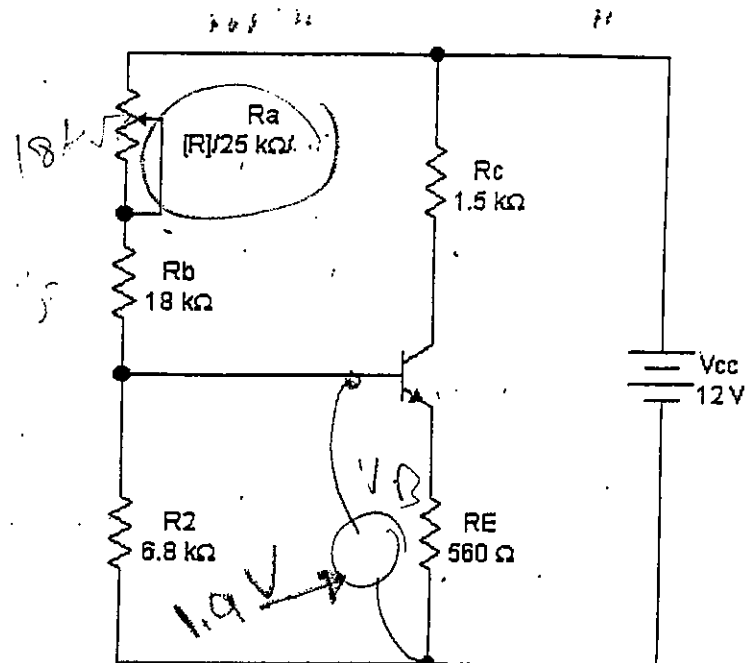


Figure 6.1

Measurements	Computer Simulation	Experimental		Calculation
		$R_a=18\text{ k}$	$V_B(\text{set})$	
$V_B$				1.9
$V_E$				
$V_{BE}$				
$V_C$				
$V_{CE}$				
$I_E$				

Table 6.1

## Part II (Computer Simulation)

## Procedure:

- 1- Setup the circuit of Figure 6.1 using (Electronics Workbench Software).
- 2- Setup  $R_a$  to 18 kΩ.
- 3- Measure the points indicated in Table 6.1 and record under computer simulation column.

**Part III (Calculation)****Procedure:**

- 1- With  $R_1$  equals  $18\text{ k}\Omega$ , calculate  $V_B$ .
- 2- Calculate  $I_B$  and  $I_C$ .
- 3- Calculate the rest of the points, record in Table 6.1 under calculation column.

**Report:**

- 1- Compare between the columns of measurement, verify the changes if there is any.
- 2- Write brief conclusion about the advantages of the circuit.

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2}$$

$$V_E = V_B - V_{BE} = 3.2 - 0.7$$

$$V_{CE} = V_{CC}$$

$$-12 + I_C R_C + V_{CE} + I_E R_E = 0$$

$$12 - 6.93 - (4.6 \times 560) \neq V_{CC}$$

2.576

## Experiment No. (7) Impedance, Power, and Phase Relationship of A Common-Emitter Amplifier

### Objectives:

To become familiar with the measure of power gain, input and output impedance and investigate the phase relationship between the output and input signals of a common-emitter amplifier.

### Theoretical Background:

The common-(ground)-emitter amplifier has been described as a power amplifier. Power can be computed from the equation  $P = V^2/R$ . The input power of CE amplifier is  $P_{IN} = V_{IN}^2/R_{IN}$ . The output power is  $P_{out} = V_{out}^2/R_{out}$ . To determine  $R_{IN}$  and  $R_{out}$ . A method for determining  $R_{IN}$  is shown in Figure 7.1. Figure 7.1(a) shows the standard input circuit, Figure 7.1(b) we have added a variable resistance (potentiometer).

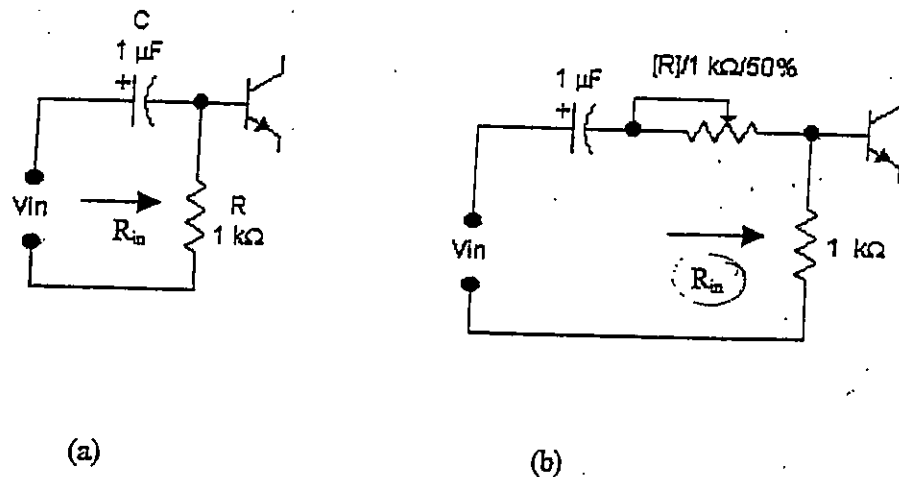


Figure 7.1

First, we set the potentiometer to zero and adjust  $V_{IN}$  until we have an easily measured value of  $V_{OUT}$ . Then we adjust the potentiometer until the output voltage is exactly one-half. We have a voltage divider on the input. Half the voltage is dropped across the potentiometer. The other half is dropped across  $R_{IN}$ . Therefore,  $R_{IN}$  must be equal to the resistance value we have set on the potentiometer. We then remove the potentiometer from the circuit and measure its value with an ohmmeter. This gives us the value of  $R_{IN}$ .

A similar thing is done to measure  $R_{OUT}$ .

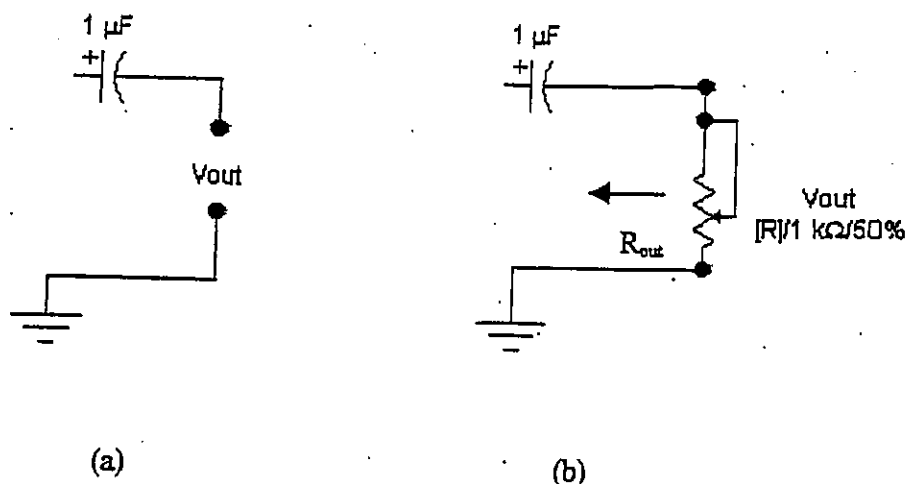


Fig 7.2.



Again we have a voltage divider made up of  $R_{OUT}$  and the potentiometer. First, without the potentiometer Fig 7.2 (a); we set the output to some value, then we put the potentiometer across the output as shown in Fig 7.2 (b) and adjust its resistance until the output is exactly one-half that previously measured. Again remove the

potentiometer from the circuit and measure its resistance, this is the output impedance  $R_{OUT}$ .

Power gain given by the equation:  $P = P_{OUT} / P_{IN}$ . This can be computed by substituting  $V^2/I$  for  $P$ .

Rather than express power gain as the absolute ratio of  $P_{OUT}$  to  $P_{IN}$ , it is usually expressed in decibels.

Power gain in decibels =  $10 \log (P_{OUT} / P_{IN})$ .

In a CE amplifier, the output signal voltage is  $180^\circ$  out of phase with the input signal voltage at the base.

This relationship is easy to keep in mind when we remember how transistors perform a switching function. With 0 input at the base, the transistor does not conduct. Therefore, virtually the entire  $V_{CC}$  appears across the output. When a signal is put on the base so as to drive the transistor into saturation, it conducts for the full cycle and the voltage across it is zero.

### Materials and Equipment:

- 1 DC power supply
- 1 AF signal generator
- 1 Oscilloscope
- 1 AVO meter
- 1 Resistor, 560 ohm
- 1 Resistor, 1k ohm
- 1 Resistor, 8.2k ohm
- 1 Resistor, 18k ohm
- 1 Capacitor, 100  $\mu F$
- 2 Capacitors, 25  $\mu F$
- 1 Transistor, 2N3904(# 571)
- 1 Potentiometer, 1k ohm
- 1 Potentiometer, 5k ohm
- 1 Computer (with Electronic Workbench software)

### PART I (Experimental)

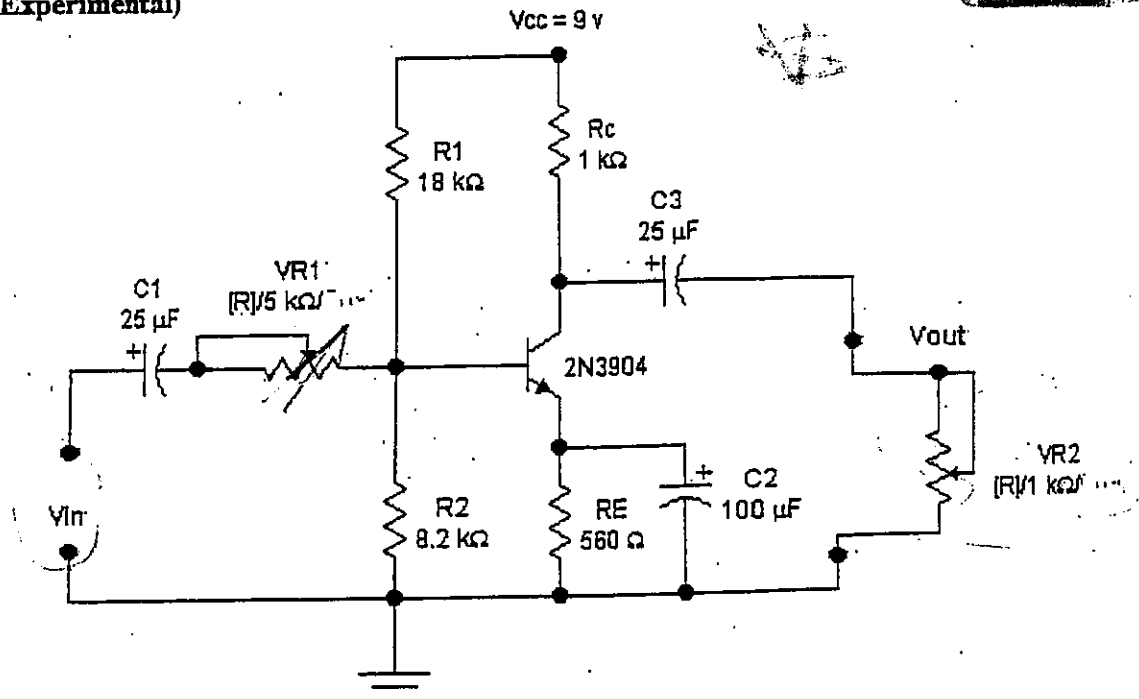


Figure 7.3

Procedure:

- 1- a) Connect the circuit of Figure 7.3.  
b) Measure  $I_C$ ,  $I_E$ , and  $I_B$ , record to be used in the calculation part.
- 2- a) Set the  $5k\ \Omega$  potentiometer to zero ohms.  
b) Set the signal generator for 1 kHz and apply its output to  $V_{IN}$ .  
c) Set the oscilloscope to view  $V_{OUT}$ .
- 3- Turn ON the power and adjust the output signal generator until  $V_{OUT}$  reads 6 volts peak-to-peak on the oscilloscope.
- 4- Increase the resistance of the potentiometer until the output voltage is exactly 3 volts peak-to-peak.
- 5- a) Turn off the power and the signal generator.  
b) Remove the potentiometer from the circuit and without changing its setting, measure its resistance.  
c) Record this as  $R_{IN}$  in Table 7.1.
- 6- a) Put a lead in the circuit in place of the input potentiometer.  
b) Turn ON the signal generator.  
c) Repeat step 3.
- 7- Connect the  $1k\ \Omega$  potentiometer across the output terminals, as shown in Fig 7.3.
- 8- Adjust the potentiometer until the output voltage is exactly 3 volts peak-to-peak.
- 9- a) Turn OFF the power and the signal generator.  
b) Remove the potentiometer from the circuit and without changing its setting, measure its resistance.  
c) Record this as  $R_{OUT}$  in Table 7.1.
- 10- Turn ON the power, with the signal generator still set to 1 kHz, adjust its output until the output voltage of the amplifier reads 6 volts peak-to-peak.
- 11- Measure the input voltage (peak-to-peak) and record the value of  $V_{IN}$  in Table 7.1.
- 12- a) With the same setting as in step 11 connect a load resistor of  $1k\ \Omega$  across the output terminal.  
b) Measure the output voltage ( $V_O$ ) w/L record in Table 7.1.

## PART II (Computer Simulation)

## Procedure:

- 1- Set up the circuit of Figure 7.3 using (Electronics Workbench Software).
- 2- Go through the same procedure as you did in your experimental part from step 2 to step 11.
- 3- Under analysis Menu go for AC frequency analysis.
- 4- Select 1Hz as start frequency and 10 GHz as end frequency, do not forget to select the proper nodes the input and the output.
- 5- Observe the frequency response and the phase angle, record in Table 7.1.

Measurements	Computer Simulation	Experimental	Calculation
Input Impedance $R_{IN}$ (ohms) ✓			
Output Impedance $R_{OUT}$ (ohms) ✓			
Input Voltage $V_{IN}$ (p-p) ✓			
Output Voltage $V_{OUT}$ (p-p) ✓			
Output Voltage $V_{OUT}(p-p)_{w/L}$			
Voltage Gain $A_V$			
Voltage Gain $A_{Vw/L}$			
Power Gain $A_P \approx \frac{P_o}{P_i}$			
Power Gain (dB) $PG_{dB}$			
Phase angle (degree)			

Table 7.1

## PART III (Calculation)

- 1- Use the measured data in step 1 (b) in the experimental part to calculate  $\beta$ , and  $r_e$ .
- 2- Draw the equivalent ac model.
- 3- Calculate the input and output impedances  $R_{IN}$  and  $R_{OUT}$ .
- 4- Calculate the voltage gain  $A_V$  and the current gain  $A_i$ .

## REPORT:

- 1- Compare between the data in the three columns in Table 7.1.
- 2- Under data analysis in your report, write your opinion about step 1 of the report section.
- 3- Write what you have concluded from this experiment.

## Experiment No. (8) The Emitter Follower

### Objective:

To become familiar with the common-collector amplifier, also known as emitter follower.

### Theoretical Background:

The common-emitter amplifier had voltage, current and power gain. The common-collector amplifier, on the other hand, has only current and power gain. The voltage gain is a little less than 1. The common-collector amplifier has high input impedance and low output impedance, however, making it ideal for impedance matching applications, known as buffer stage.

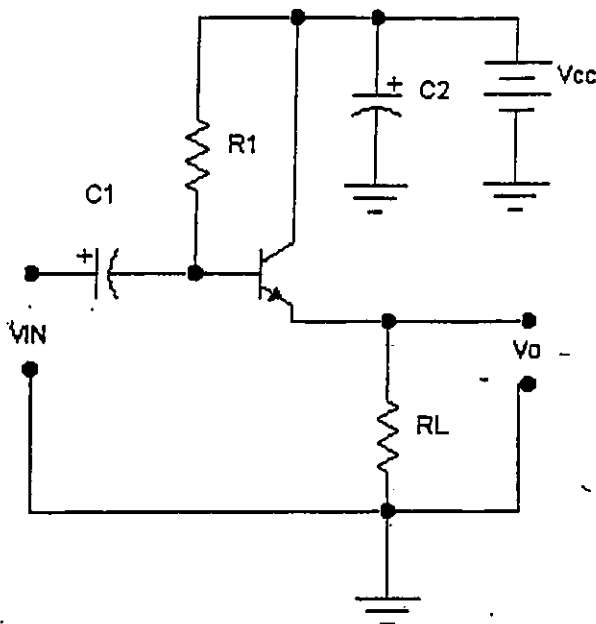


Fig 8.1

Figure 8.1 shows a common-emitter amplifier, the input signal  $V_{IN}$ , is coupled to the base through capacitor  $C_1$ . The load resistor, across which  $V_O$  is taken, is connected to the emitter. Note that the collector is at AC ground because capacitor  $C_2$  acts as a low-impedance AC path. The collector is connected directly to  $V_{CC}$ . The input signal,  $V_{IN}$ , appears between base and ground (collector), and the output signal appears between emitter and ground (collector). This makes the collector common to both input and output.

Consider what happens when  $V_{IN}$  increases during a positive AC alternation. Both the collector current and the emitter current increase. Emitter voltage  $V_O = I_E R_L$ , therefore, becomes more positive. In other words, when  $V_{IN}$  goes positive,  $V_O$  (emitter voltage) follows. This is why this amplifier is called an emitter follower. Note that  $V_O$  is in phase with  $V_{IN}$ .

The base current,  $I_B$ , is amplified by a factor of  $\beta$ . Output current, then is  $\beta I_B$ . We can look upon this as two loop that have  $R_L$  as a common leg and write Kirchhoff's voltage law equation. One loop (neglecting  $C_1$ ) is made up of the source,  $V_{IN}$ ; the base-to-emitter resistance,  $R_B$ , through which  $I_B$  flows) and the resistance,  $R_L$  (through which  $I_B + \beta I_B$  flows). Therefore,

$$V_{IN} = I_B R_B + I_B R_L + \beta I_B R_L$$

$$V_{IN} = I_B (R_B + R_L + \beta R_L)$$

$$V_{IN} = I_B (R_B + R_L (\beta + 1))$$

New, let's look at the second loop, make up the output voltage,  $V_O$ , and the resistance,  $R_L$ , (through which  $I_B + \beta I_B$  flows):

$$V_O = I_B R_L + \beta I_B R_L$$

$$V_O = I_B R_L (\beta + 1)$$

We can, therefore, substitute in the equation for voltage gain,  $A_V = V_O / V_{IN}$ .

$$A_V = \frac{I_B R_L (\beta + 1)}{I_B (R_B + R_L (\beta + 1))} \quad \text{The } I_B \text{'s cancel}$$

$$A_V = \frac{R_L (\beta + 1)}{R_B + R_L (\beta + 1)}$$

For example, assume the following values:  $\beta = 99$ ;  $R_L = 1000$  ohms,  $R_B = 2000$  ohms.

$$A_V = \frac{1000 \times (99 + 1)}{2000 + 1000 \times (99 + 1)} = 0.98$$

Without  $R_L$ ,  $V_{IN}$  would be simply  $I_B R_B$ . We saw, however, that the effective value of the input impedance was increased with the addition of  $R_L$ . In fact, it becomes  $R_B + R_L (\beta + 1)$ . In our example, instead of 2000 ohms, the input impedance was a 102000 ohms.

Since the phase of signal voltage (emitter-to-ground) is the same as the base voltage (base-to-ground), and since the input signal voltage to the circuit is the difference between the base voltage and emitter voltage, the effect of the un-bypassed emitter resistor is to provide degenerative, or negative, feedback to the circuit. In other words, the amplifier sees a lower effective input signal between base and emitter than  $V_{IN}$ .

#### Materials equipment:

- 1 DC Power Supply
- 1 AF Signal Generator
- 1 Oscilloscope
- 1 AVO meter
- 1 Resistor, 1 k ohms
- 1 Resistor, 470 k ohms
- 1 Capacitor, 25  $\mu$ F
- 1 Capacitor, 100  $\mu$ F
- 1 Transistor, 2N2102
- 1 Potentiometer, 1 k ohm
- 1 Potentiometer, 500 k ohm

#### Part I (Experimental)

##### Procedure:

- 1- Connect the circuit of Figure 8.2 with  $R_{V1}$  set to zero ohms.
- 2- Measure  $I_B$  and  $I_C$ , to be used in part III (calculation).

3- a- Set the Signal Generator for 1000 Hz.

b- Apply power to the circuit.

c- Connect the output of the Signal Generator to the input of the circuit, with no load ( $R_{V2}$  disconnected).

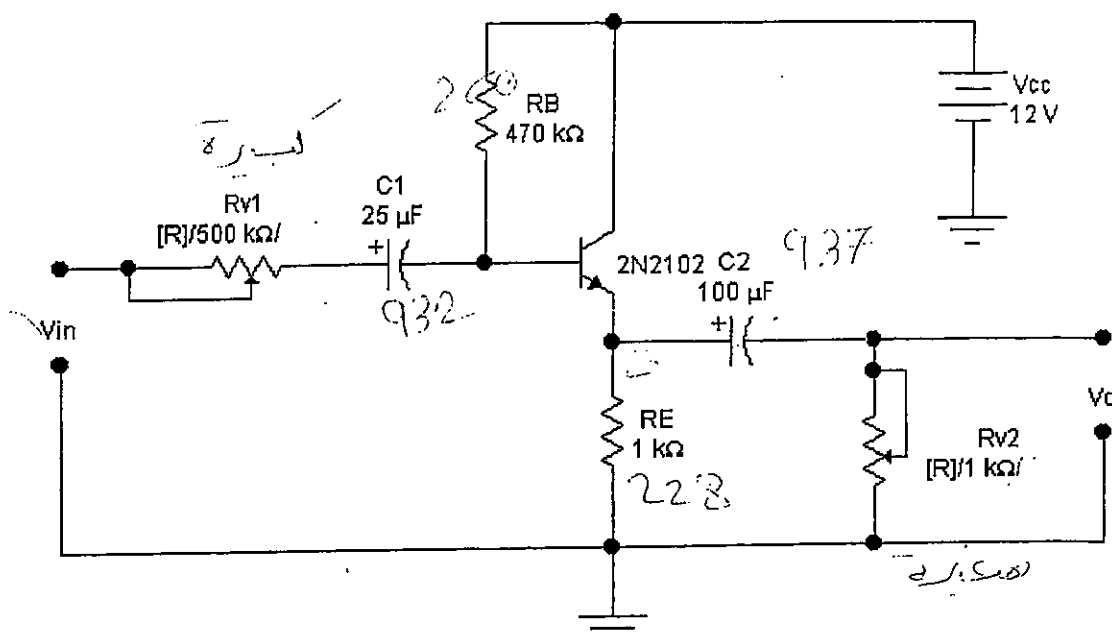


Fig 8.2

4- a- Connect the Oscilloscope to the output terminals to observe  $V_o$ .

b- Set the Signal Generator to a value that produces an undistorted output waveform measuring 150 V peak-to-peak.

5- Measure the peak-to-peak value of  $V_{IN}$  and record in Table 8.1.

6- Adjust the 500-k ohm potentiometer until the output waveform measures exactly 75 mV peak-to-peak.

7- a-Switch off the power.

b- Disconnect the potentiometer from the circuit.

c- Measure its resistance and record as  $R_{IN}$  in Table 8.1.

8- a- Replace the 500 k ohm potentiometer by a wire.

b- Repeat step 3.

c- Connect the 1 k ohm potentiometer in parallel with the output.

d- Adjust it until the output measures exactly 75 mV peak-to-peak.

e- Disconnect from the circuit, measure its value and record as  $R_{OUT}$  in Table 8.1

(آرودیٹ)

CC :

\* common collector

$$AV \leq 1$$

collector common bet  $I \neq 0$

Ac model  $\rightarrow$  collector  $\rightarrow$

موصول  
بالتطابق

Ac model  
نقص جبرادند

I ناخذہ  
B

لٹ

مشترک

لٹ 0 ناخذہ E

المشترک C بی  $I \neq 0$

voltage

We can't use as amplifier  
but we can use as current amp  
because  $AV \leq 1$

$$V_O = V_i$$

we use it in impedance  
matching application

یربط بین دائرتین


Ac  $\rightarrow$  capacitor  $\rightarrow$  short-circuit

- 9- Use your measurements, calculate voltage gain  $A_v$ , input power, and output power record in Table 8.1.
- 10- Using the data in step 9 calculate the power gain  $A_p$ .

## Part II (Computer Simulation)
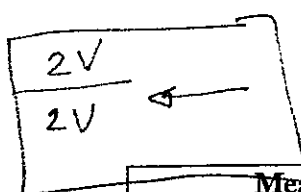
### Procedure:

- 1- Set up the circuit of Figure 8.2 using (Electronics Workbench Software), make shore that the 500-k ohm potentiometer is set to zero ohm.
- 2- Go through the same procedure as you did in your experimental part from step 3 to step 10.
- 3- Under Analysis menu go for AC frequency analysis, select 1 Hz as start frequency and 10 GHz as end frequency, do not forget to select the proper nodes (the input and the output).
- 4- Observe the frequency response and the phase angle, record in Table 8.1.



Handwritten calculations and notes:

$$V_i = 150 \text{ mV}$$

$$V_o = 150 \text{ mV}$$

$$R_i = 51 \text{ k}$$

$$R_o = 22.4 \text{ } \Omega$$

$$R_o \rightarrow \infty$$

$$R_{in} \rightarrow \infty$$

$$I_E = 1.1 \text{ mA}$$

$$I_B = 0.02 \text{ mA}$$

$$I_C = 1.08 \text{ mA}$$

Measurements	Computer Simulation	Experimental	Calculation
Output voltage ( $V_o$ )	150 mV <sub>P-P</sub>	150 mV <sub>P-P</sub>	
Input voltage ( $V_{IN}$ )	150 mV		
Voltage gain ( $A_v$ )	1		$V_o/V_i$
Input impedance ( $R_{IN}$ )	100k $\rightarrow$ 200k	50k $\Omega$	
Output impedance ( $R_{OUT}$ )	40 $\Omega$	400 $\Omega$	
Input power ( $P_{IN}$ ) = $V_{IN}^2 / R_{IN}$	$1.406 \times 10^{-7}$		
Output power ( $P_{OUT}$ ) = $V_{OUT}^2 / R_{OUT}$	0.0005825		
Power gain ( $A_p$ ) = $P_{OUT} / P_{IN}$	4000.7		

## Part III (Calculation)

- 1- Using the measured data in step 2 in the experimental part to calculate  $\beta$ , and re.  $L$
- 2- Draw the equivalent ac model.
- 3- Calculate the input and output impedance  $R_{IN}$ , and  $R_{OUT}$ .
- 4- Calculate the voltage gain  $A_v$ , and the current gain  $A_i$ .

## REPORT:

- 1- To how extend computer simulation, experimental, and calculation results are identical.
- 2- Write what you have concluded from this experiment.

Handwritten calculations and notes:

$$150 \text{ mV} = V_i$$

$$150 \text{ mV} = V_o$$

$$R_{in} = 51 \text{ k}$$

$$R_o = 22.4 \text{ } \Omega$$

$$I_E = 1.1 \text{ mA}$$

$$I_B = 0.02 \text{ mA}$$

$$I_C = 1.08 \text{ mA}$$



$$R = \frac{I_C}{I_B} \quad r_e = \frac{26mV}{I_{E_{measured}}}$$

$$Z_i = R_B \parallel B C r_e \parallel R_E \quad \begin{matrix} \downarrow 470K\Omega & \rightarrow 1K\Omega \end{matrix}$$

$$A_v = \frac{R_E}{r_e + R_E} \approx 1$$

$$A_i = \frac{-\beta R_B}{R_B + \beta(r_e + R_E)}$$

$$Z_o = r_e \parallel R_E \approx r_e$$

$$\beta = \frac{I_C}{I_B}$$

$$r_e = \frac{26mV}{I_E}$$

$$I_E = 1.016mA \quad I_C = 1.014mA \quad I_B = 0.02mA$$

$$\beta = \frac{I_C}{I_B} = \frac{1.014}{0.02} = 50.7$$

$$r_e = \frac{26mV}{1.016mA} = 25.6 \quad \leftarrow \underline{RD}$$

$$Z_i = 470K \parallel 50.7 (25.6 \cdot 1 + 1000)$$

$$470K \parallel 53 \quad \frac{470 \times 53}{470 + 53} = 47.25K$$

CC  
 \* common collector  $AV \leq 1$   
 collector common bet  $I \neq 0$

Ac model  $\rightarrow$  collector  $\rightarrow$  موصول یا بطاریه  
 Ac model " نظیر جبرادین

نظیر مشترک لٹ I ناخذہ  
 B

لٹ 0 ناخذہ E

المستترک C بی I  $\neq 0$   
 voltage

We can't use as amplifier  
 but we can use as current amp  
 because  $AV \leq 1$   $V_O = V_i$

we use it in impedance  
 matching application

یربط بیر (دائریتا)

Ac  $\rightarrow$  capacitor  $\rightarrow$  seho short-circuit

3- a- Set the Signal Generator for 1000 Hz.

b- Apply power to the circuit.

c- Connect the output of the Signal Generator to the input of the circuit, with no load ( $R_{V2}$  disconnected).

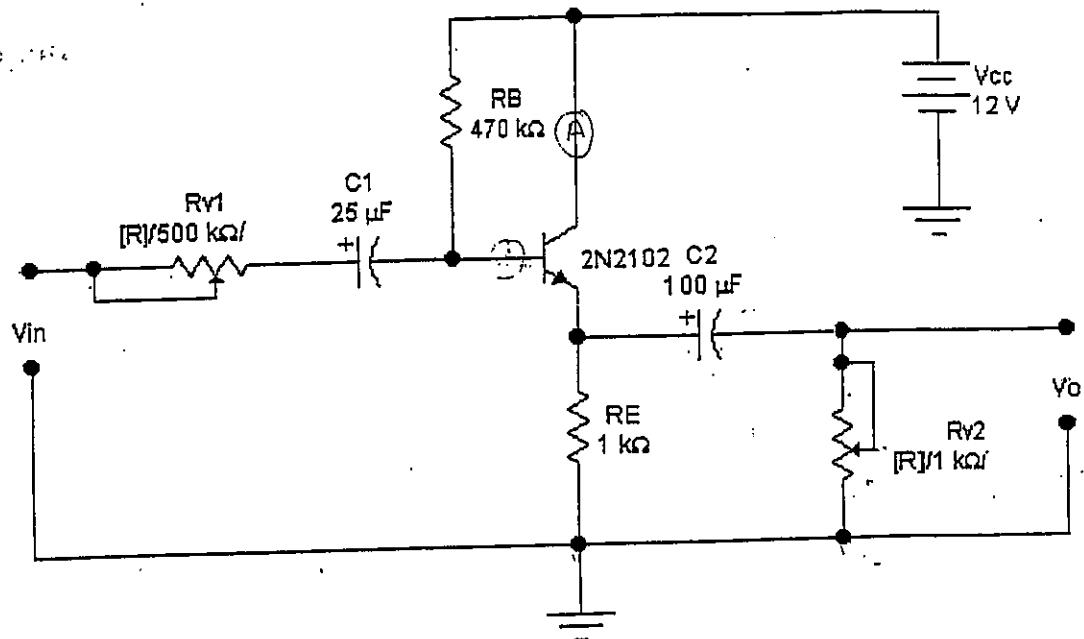


Fig 8.2

4- a- Connect the Oscilloscope to the output terminals to observe  $V_o$ .

b- Set the Signal Generator to a value that produces an undistorted output waveform measuring 150 mV peak-to-peak.

5- Measure the peak-to-peak value of  $V_{IN}$  and record in Table 8.1.

6- Adjust the 500-k ohm potentiometer until the output waveform measures exactly 75 mV peak-to-peak.

7- a- Switch off the power.

b- Disconnect the potentiometer from the circuit.

c- Measure its resistance and record as  $R_{IN}$  in Table 8.1.

8- a- Replace the 500 k ohm potentiometer by a wire.

b- Repeat step 3.

c- Connect the 1 k ohm potentiometer in parallel with the output.

d- Adjust it until the output measures exactly 75 mV peak-to-peak.

e- Disconnect from the circuit, measure its value and record as  $R_{OUT}$  in Table 8.1

- 9- Use your measurements, calculate voltage gain  $A_v$ , input power, and output power record in Table 8.1.
- 10- Using the data in step 9 calculate the power gain  $A_p$ .

### Part II (Computer Simulation)

#### Procedure:

- 1- Set up the circuit of Figure 8.2 using (Electronics Workbench Software), make shore that the 500-k ohm potentiometer is set to zero ohm.
- 2- Go through the same procedure as you did in your experimental part from step 3 to step 10.
- 3- Under Analysis menu go for AC frequency analysis, select 1 Hz as start frequency and 10 GHz as end frequency, do not forget to select the proper nodes (the input and the output).
- 4- Observe the frequency response and the phase angle, record in Table 8.1.

Measurements	Computer Simulation	Experimental	Calculation
Output voltage ( $V_O$ )	150 mV <sub>P-P</sub>	150 mV <sub>P-P</sub>	
Input voltage ( $V_{IN}$ )			
Voltage gain ( $A_v$ )			
Input impedance ( $R_{IN}$ )			
Output impedance ( $R_{OUT}$ )			
Input power ( $P_{IN}$ ) = $V_{IN}^2 / R_{IN}$			
Output power ( $P_{OUT}$ ) = $V_{OUT}^2 / R_{OUT}$			
Power gain ( $A_p$ ) = $P_{OUT} / P_{IN}$			

Table 8.1

### Part III (Calculation)

- 1- Using the measured data in step 2 in the experimental part to calculate  $\beta$ , and  $r_e$ .
- 2- Draw the equivalent ac model.
- 3- Calculate the input and output impedance  $R_{IN}$ , and  $R_{OUT}$ .
- 4- Calculate the voltage gain  $A_v$ , and the current gain  $A_i$ .

#### REPORT:

- 1- To how extend computer simulation, experimental, and calculation results are identical.
- 2- Write what you have concluded from this experiment.

## Experiment No. (9) JFET Common-Source Amplifier

### Objective:

To gain an understanding of the JFET common-source amplifier.

### Theoretical Background:

The common-source amplifier, which we have been using, is the most common type of JFET amplifier. It is also called a ground-source amplifier because the source end of the circuit is common to both the input and output and is at the lowest voltage of any point in the circuit.

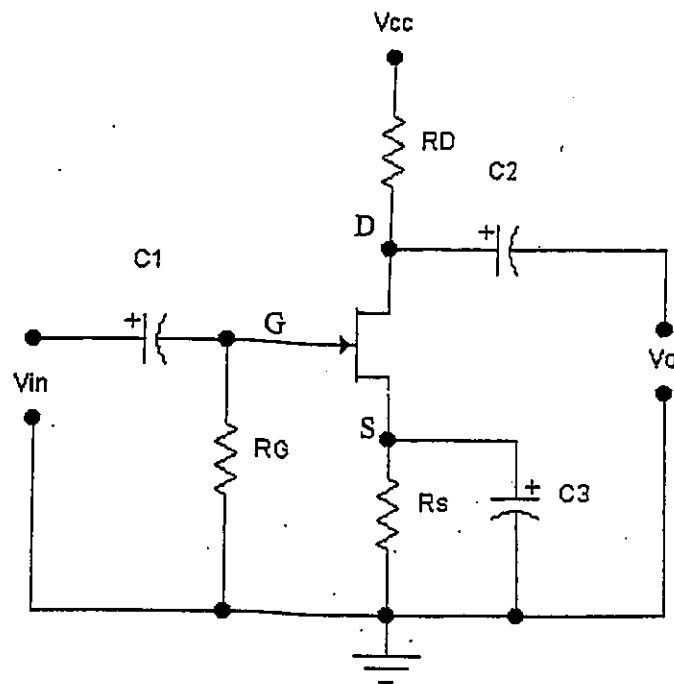


Figure 9.1

Figure 9.1 shows a common-source amplifier. To isolate the gate from the source, the input signal,  $V_{in}$  is coupled to gate through capacitor  $C_1$ . The value of the capacitor is chosen to present a very low reactance to signals in the frequency range over which it is to operate.

A load resistor in series with the drain  $R_D$ , provides a means of limiting drain-to-source voltage to a pre-determined value. The gate resistor is usually quite large. The exact value isn't important, as long as it is large enough not to short out the input signal. Its purpose is to tie the gate to ground. Since no current flows in the gate circuit as long as the gate is negative ( $-V_{GS}$ ) there is no voltage drop across  $R_G$ . one end of it has the same DC potential as the other.


Current does flow through  $R_S$ , however from the positive terminal of the supply, through  $R_D$ , through the JFET, through  $R_S$  and back to the negative terminal. That makes the top end of  $R_S$  more positive than the bottom end. Since the gate is effectively connected to the bottom end of  $R_S$ , the gate is more negative than the source. This is just what we need for a negative bias on JFET gate.

The common-source amplifier has high input impedance, high output impedance, and good voltage gain.

## Materials and Equipment:

- 1- DC Power supply.
- 1- AF Signal Generator.
- 1- AVO meter.
- 1- N-channel JFET 2N5459.
- 1- Resistor, 390 ohm.
- 1- Resistor, 390 ohm.
- 1- Potentiometer, 1 k ohm.
- 2- Capacitor, 0.05  $\mu$ F.
- 1- Capacitor, 25  $\mu$ F.

2N5459

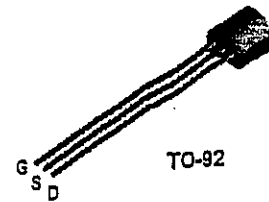

## N-Channel General Purpose Amplifier

Part I (Experimental)  
Procedure:

- 1- Identify the JFET terminals.
- 2- Connect the circuit of Figure 9.2.
- 3- Set  $R_S$  initially to 300  $\Omega$ , to measure the value of  $g_m$  for a JFET.

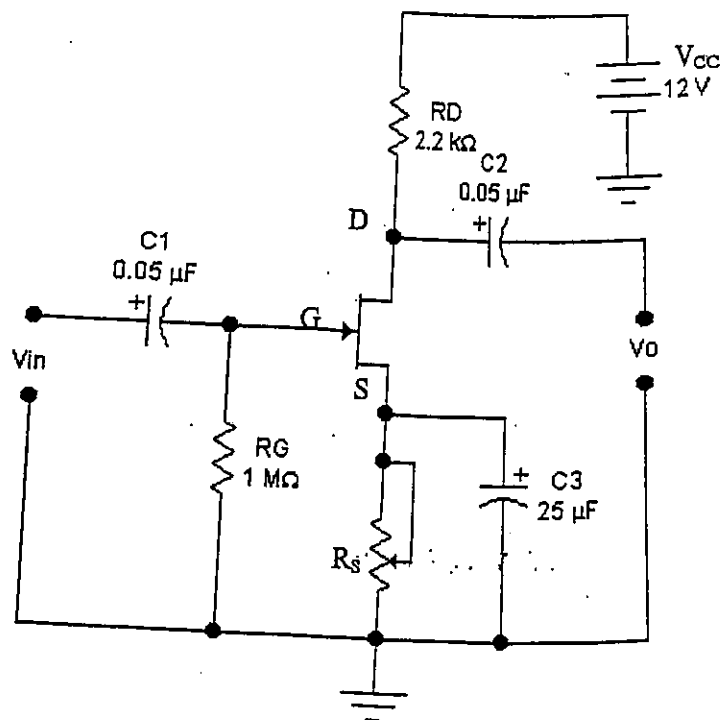


Figure 9.2

- 4- With  $R_S$  set to 300  $\Omega$ , measure  $V_{GS}$ ,  $I_D$  and record in Table 9.1.
- 5- Adjust  $R_S$  to a value of 400  $\Omega$ , and measure  $V_{GS}$ ,  $I_D$  again and record in Table 9.1.

- 6- Using your data calculate the amplifier gain  $A_v$

$$A_v = g_m R_D$$

*****	Experimental $R_s$		Computer Simulation $R_s$	
Measurement	300 $\Omega$	400 $\Omega$	300 $\Omega$	400 $\Omega$
$V_{GS}$				
$I_D$				

Table 9.1

- 7- Switch the power off, replace the 1 k $\Omega$  potentiometer with 390  $\Omega$  fixed resistor.
- 8- With the AVO meter, measure and record in Table 8.2 the DC drain-to-ground voltage,  $V_D$ .
- 9- Measure and record in Table 9.1 the DC voltage drop across the 390  $\Omega$  source resistor,  $V_{RS}$ .
- 10- Measure and record in Table 9.1 the DC bias voltage from gate-to source,  $V_{GS}$ .
- 11- Turn on the signal generator and set it for 1000 Hz at 1 volt peak-to-peak.
- 12- Measure the peak-to-peak value of the output signal  $V_O$ , record in Table 9.2.
- 13- Calculate the amplifier gain using the equation  $A_v = V_O/V_{in}$  record your result in Table 9.2.
- 14- Adjust the vertical sensitivity of your oscilloscope channels so that you can observe both the input and output waveforms on the CTR at the same time. Then neatly draw the two waveforms in their proper phase relationship.

Measurement	Computer Simulation	Experimental	Calculation
$V_D(DC)$			
$V_{RS}(DC)$			
$V_{GS}(DC)$			
$V_{in}(p-p)$	1 V	1 V	1 V
$V_O(p-p)$			
GAIN $A_v = V_O/V_{in}$			
GAIN $A_v = g_m R_D$			

Table 9.2

**Part II (Computer Simulation)****Procedure:**

- 1- Set up the circuit of Figure 9.2 using (Electronics Workbench Software).
- 2- Go through the same procedure as you did in the experimental part from step 2 to 14.
- 3- Under analysis menu go for AC frequency analysis.
- 4- Select 1 Hz as start frequency and 100 MHz as end frequency.
- 5- Observe the frequency response and the phase angle.

**Part III (Calculation)**

- 1- Given  $I_{DSS} = 6 \text{ mA}$ , and  $V_P = -3 \text{ V}$ , draw the transfer characteristics for the JFET.
- 2- Determine  $I_D$ , and  $V_{GS}$ .
- 3- Draw the equivalent AC model for the circuit of Figure 9.2.
- 4- Calculate  $R_{in}$ , and  $R_{out}$ .
- 5- Calculate  $I_D$ ,  $V_D$ ,  $V_{RS}$ ,  $V_{GS}$ , and the gain  $A_v$ .

**Report:**

- 1- To how extent the columns of Table 9.2 are identical.
- 2- Under data analysis in your report, write your opinion about step 1.
- 3- Write what you have concluded from this experiment.



## Experiment No. (10) JFET COMMON-DRAIN AMPLIFIER

### Objective:

To investigate the operation of a common-drain JFET amplifier.

### Theoretical Background:

The common-drain amplifier is also called a source-follower. In many ways, it is similar to the emitter-follower circuit of the bipolar transistor. Like the common-source, the source follower has high input impedance. Unlike the common-source amplifier, however, its input impedance is relatively low and its voltage gain is always less than 1. It is mainly used as an impedance matching device.

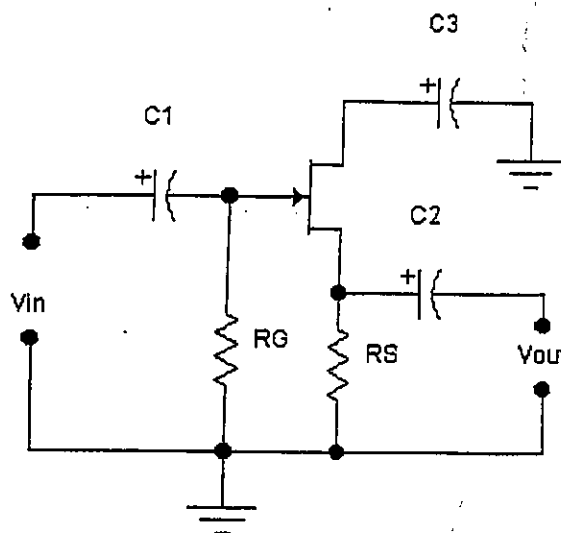


Figure 10.1

In a source-follower amplifier, the output signal appears across  $R_S$  as shown in Fig 10.1. Naturally, this means that the bypass capacitor must be eliminated. Going around the loop composed of  $R_G$ , the JFET, and  $R_S$ , it becomes obvious that:

$$V_{RS} \text{ (the output voltage)} = V_{RG} \text{ (the input voltage)} - V_{GS}$$

That's why the output voltage,  $V_O$  must be less than the input voltage,  $V_{IN}$ .

As before, the value of  $R_S$  sets the gate bias voltage. It is also true that the higher the value of  $R_S$ , the closer the gain approaches 1. Therefore, a voltage divider is used so that  $R_S$  can be made larger.

The input impedance of a JFET source-follower amplifier is high. It is kept high value of  $R_G$ . The higher the resistance, the greater the effect. However, if the gate resistance is returned to the voltage divider instead of to ground, the input impedance looks much higher than  $R_G$  to the preceding stage. In fact, what the preceding stage sees is  $R_G$  in series with the parallel combination of the two biasing resistors ( $R_1$  and  $R_2$ ).

Also, looking back from the load, the output impedance is seen much lower than the value of  $R_S$ . Since the drain is common, the reciprocal of the transconductance ( $1/g_m$ ) looks like a resistance in parallel with  $R_S$ . If you assume a transconductance of 2500 micromhos, the reciprocal is 400 ohms. Assuming  $R_S = 1000$  ohms, the load sees an output impedance of:

$$Z_{OUT} = 1/g_m \parallel R_S = 400 \parallel 1000 = 286 \text{ ohms.}$$

**Material and Equipment:**

- 1 DC Power Supply
- 1 AF Signal Generator
- 1 Oscilloscope
- 1 AVO meter
- 1 n-channel JFET, 2N5459
- 1 Resistor, 4.7 ohm
- 1 Resistor, 8.2 ohm
- 1 Resistor, 10 k ohm
- 1 Resistor, 33 k ohm
- 3 Capacitor, 0.05  $\mu$ F
- 1 Capacitor, 1  $\mu$ F

**Part I (Experimental)****Procedure:**

- 1- Connect the circuit of Figure 10.2.
- 2- Apply a 20 volts DC to the circuit.
- 3- Measure and record in Table 10.1, the DC voltage drop across each of the resistors, the drain-to-source voltage,  $V_{DS}$ , and the gate-to-source voltage,  $V_{GS}$ , of the JFET.

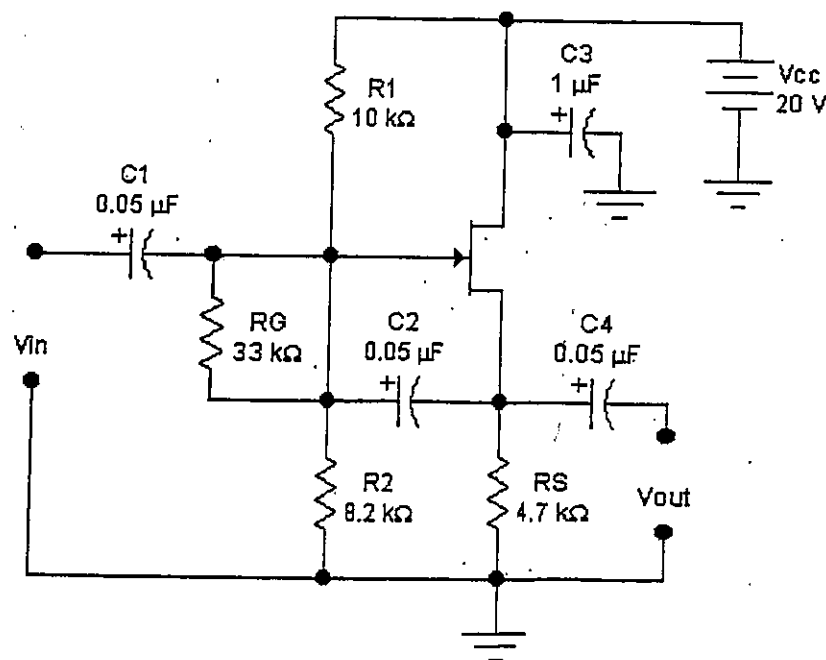


Fig 10.2

- 4- Set the Signal Generator to 1000 Hz at 1 volt peak-to-peak.
- 5- Connect the Signal Generator to the input terminals.
- 6- Measure the peak-to-peak value of the output,  $V_{OUT}$ . Record in Table 10.1.
- 7- Set your Oscilloscope for external triggering. With the scope triggered from the output of the Signal Generator, observe the waveform of the output signal. Record in table 10.1 the degrees that the output signal has shifted from the input signal.

Measurements	Computer Simulation	Experimental	Calculation
$V_{R1}$ (DC)			
$V_{R2}$ (DC)			
$V_{RG}$ (DC)			
$V_{RS}$ (DC)			
$V_{DS}$ (DC)			
$V_{GS}$ (DC)			
$V_{IN}$ (p-p)			
$V_{OUT}$ (p-p)			
Gain $A_v = V_o/V_i$			
Degrees Shift			

Table 10.1

**Part II (Computer Simulation)****Procedure:**

- 1- Setup the circuit of Figure 10.2 using (Electronics Workbench Software).
- 2- Go through the same procedure as you did in the experimental part from set 1 to step 7.
- 3- Under analysis menu go for AC frequency analysis.
- 4- Set 1 Hz as start frequency and 1 GHz as end frequency.
- 5- Observe and record the frequency response and the phase shift.

**Part III (Calculation)**

- 1- Given  $g_m = 2500$  micromhos,  $I_{DSS} = 6$  mA and  $V_p = -3$  V, draw the transfer characteristics for the JFET.
- 2- Determine  $I_D$  and  $V_{GS}$ .
- 3- Draw the equivalent AC model for the circuit of Figure 10.2.
- 4- Calculate  $R_{IN}$  and  $R_{OUT}$ .
- 5- Calculate  $V_{R1}$ ,  $V_{R2}$ ,  $V_{RG}$ ,  $V_{RS}$ ,  $V_{DS}$ ,  $V_{GS}$ , and the gain.

**Report:**

- 1- Compare between the data in the three columns in Table 10.1.
- 2- Under data analysis in your report, write your opinion about step 1.
- 3- Write what you have concluded from this experiment.